

The Authoritative Magazine About High Fidelity

**STEREO
EQUIPMENT
& RECORD
REVIEWS**

AUDIO

NOVEMBER
1969
60¢

- **SPEAKER SPECIFICATIONS** ■ **MOOG MUSIC "LIVE"**
- **BUILD AN I-C TONE-CONTROL STAGE**



**HOW DISC MASTERS
ARE MADE TODAY**

PASSIVE CROSSOVER NETWORKS FOR BI-AMPLIFIER SYSTEMS

Attributes of passive speaker crossover networks vs. electronic crossovers

BLAINE B. KUIST

ELECTRONIC CROSSOVERS are getting the spot-light in a resurgence of interest in bi- and tri-amplification (high, intermediate, and low frequencies split ahead of the power amplifiers).

A lot of hi-fi buffs might be interested in an alternative that is simpler to build (2 hours), not too costly (\$50 for two channels with one crossover point), high in reliability with few components and top performance.

The alternative is the old work-horse—passive L-C filter networks.

An article about Electronic Crossovers¹, intrigued me with the potential of improved sound with bi-amplification. My hi-fi fever set in last spring after looking for a starter outfit with my teenage son. Casual looking and listening led to growing interest.

I wondered why a treble speaker like the Altec-Lansing 802-D driver and 511-B horn couldn't be teamed with a good 15-in. speaker, thus covering the whole audio range with just one crossover. By now I had eagerly waded through some of the good handbooks for hi-fi hobbyists, such as "Speaker Enclosures," by A. Badmaieff & Don Davis,² and "Hi-Fi Projects for Hobbyists, by Leonard Feldman."³

From current literature from manufacturers like Sony, Bozak, C/M Labs, and Pioneer, a tailored design (for a selected crossover frequency and cutoff slope) of an electronic crossover appeared to be a tough project for a beginner to tackle.

Fortunately, I talked to a professional audio engineer about my interests. His reaction was, "Why not use high- and low-pass filters?"

The key idea was to feed the filters from the pre-amplifier, matching the 600-ohm output impedance of the pre-amplifier with a 600-ohm input impedance of the filter. The 600-ohm output impedance of the filter was also matched and terminated by a 600-ohm resistor (in parallel with the 100-k ohm input impedance of the power amplifier). Thus the filter was matched at the input and output with 600-ohm constant impedances.

Settling on Filters

This sounded simple enough—until I tried to find the filters. A search of electronic catalogs, stores, and magazines indicated filters were readily available with 18 dB/octave cutoff slope of the constant-*k* type but would have to be special-ordered for the 12-dB slope which was desired. Perhaps these are available from some professional audio equipment suppliers but my hurried searches failed to turn them up.

So it was back to the "do-it-yourself" method which didn't disappoint me, really. AUDIO's articles on "Professional Audio Controls"⁴ had had a reference to Howard Tremaine's comprehensive handbook on *Passive Audio Network Design*.⁵ This had the practicalities of filter design and construction spelled out.

³ Alexis Badmaieff and Don Davis, "Speaker Enclosures," Sams, 1st Ed., 3rd ptg., 1967.

⁴ Leonard Feldman, "Hi-Fi Projects for Hobbyists," Sams, 1st Ed., 3rd ptg., Nov. 1966.

⁵ A. C. Davis & Don Davis, "Professional Audio Controls," AUDIO, Feb., Mar., May, 1967.

⁶ Howard M. Tremaine, "Passive Audio Network Design," Sams, 1st ptg., Feb. 1969.

Again with simplicity in mind, I focused on parallel high- and low-pass L-C filters involving the familiar networks of conventional speaker crossovers except being designed for 600 ohms instead of the usual 4-, 8-, or 16-ohm speaker voice-coil circuits.

The filter networks selected and built are described as follows:

Parallel, *m*-derived
m = 0.6 for constant impedance over 85 per cent of transmission band
Impedance in and out: 600 Ohms
Crossover frequency: 500 Hz
Attenuation at crossover: 3 dB
Slope of attenuation: 12 dB/octave

The component values are derived from these formulas:

$$L_1 = (1 + m) \frac{R_o}{2\pi f_c} \text{ Henry}$$

$$L_2 = \frac{R_o}{2\pi f_c} \text{ Henry}$$

$$C_2 = \left(\frac{1}{1 + m} \right) \frac{1}{2\pi f_c R_o} \text{ Farad}$$

$$C_3 = \frac{1}{2\pi f_c R_o} \text{ Farad}$$

Where R_o = filter characteristic impedance

f_c = crossover frequency

In rounding up material to build the filters, we found the capacitors were readily available but the inductances were another matter. With values of 191 and 305 mH needed, air-core coils were out of the question because of large size and hence large resistance. Little usable information seems to be available for constructing iron-core inductors so it was back to the catalogs. Coils with desired characteristics were rarely listed and hard to find.

¹ C. G. McProud, "How to Build a 3-Channel Electronic Crossover," AUDIO, February 1968, p. 19.

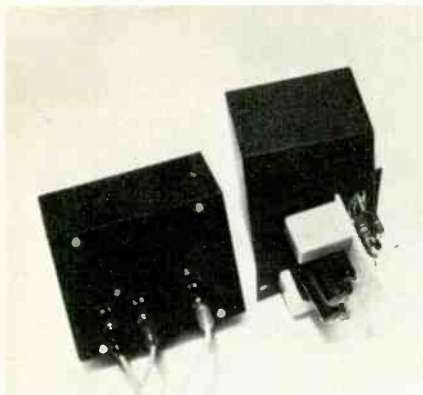


Fig. 1—The passive networks are assembled in metal boxes, and connected ahead of the power amplifiers—one for the highs, and one for the lows.

However, the United Transformer Company catalogs listed coils that covered the audio-frequency range with Q's of the order of 10 to 30 at the 500-Hz crossover point.

For the first pair of coils, the HVC Variductors were tried because they were adjustable and available at a nearby electronic store. The coils were finally set reasonably close to the desired values but they were sensitive to set, although once set, they held their settings and worked well.

For the second pair of coils, the MQA fixed inductances were chosen.

These high "Q" toroids with inductances of 200 and 300 mH \pm 1 per cent, the numbers closest to those desired without a special order. This compromise on inductance from the desired 191 and 305 mH was not significant.

A description of the coils used follows:

		<i>mH</i>	<i>d.c. mA</i>	<i>Resistance</i>
Filter A	HVC-4 Variductors	30-300	30	8.6 ohms
	HVC-5 Variductors	70-700	20	22
Filter B	MQA-8 Hi-Q Toroids	200	50	16
	MQA-9 Hi-Q Toroids	300	40	25

Typical "Q" curves for the metal-core coils rise to a peak then fall off after the saturation point of metal cores is reached. The peak Q (about 160) for the MQA coils occurs at about 5 kHz. At the crossover of 500 Hz the Q is about 40. At 20 kHz, Q is about 25 and at 20 Hz it is in the range of only 1 to 2.

The HVC coils being adjustable, the peak Q falls somewhere in the lower half of the audio range depending on the setting. At 500 Hz the Q is in the range from 5-15.

Although the MQA coil had in general the higher Q characteristics,

there was no audible difference in performance.

Filters Assembled

With the coils in hand, the remaining parts were readily available and the assembly went fast. All the parts were mounted on a plastic board fastened to the cover of a 4" x 5" x 3" steel box. Steel was used

for shielding although this was found later to be unessential.

The assembled filters are shown in the Fig. 1 with the back of the cover and the board exposed to show wiring and components for one low- and high-pass filter combination.

Response vs. frequency curves were run with an audio generator and a VTVM with the results shown in Fig. 3. The 520-Hz crossover point was close enough to the 500-Hz goal.

The crossover point was down 3.5 dB from the bass plateau and

Fig. 2—Schematic of the passive filter networks used with the bi-amplification system described by the author. Two networks are required for stereo.

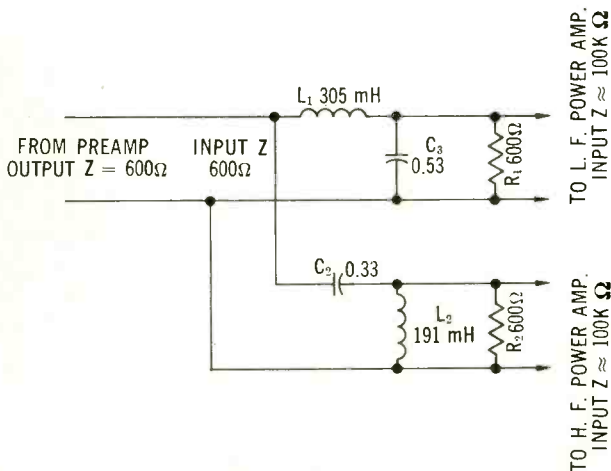


Fig. 3—Frequency-response curves for the author's passive networks.

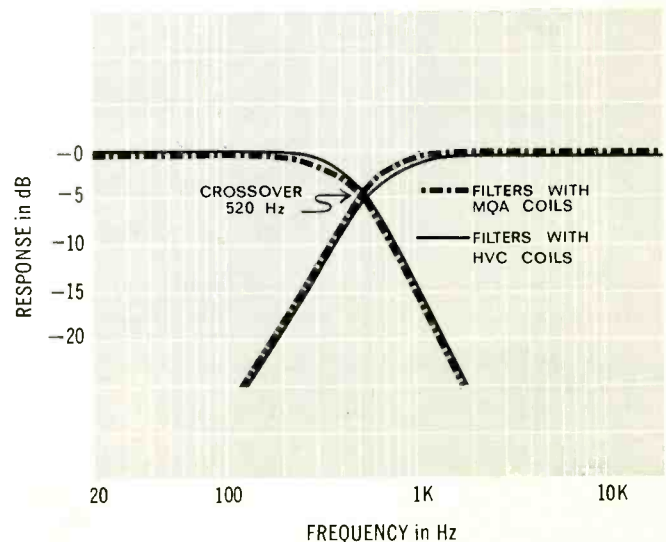


TABLE I
COMPARISON OF CROSSOVER ALTERNATIVES

	PASSIVE Ahead of Amplifiers	ELECTRONIC Ahead of Amplifiers	CONVENTIONAL After Amplifiers
Bass speaker: damping and transient response	Permits performance to full damping ability of amps.	same as passive	Reduces woofer response by resistance and reactive impedance between ampl. and speakers.
Amplifier performance	IM distortion minimized by high and low frequencies go- ing through separate ampli- fiers. Greater dynamic range due to separate amplifiers.	same as passive	IM distortion due to hi and low going through same amplifier. Dynamic range limited because power peaks for hi and low are additive.
Speaker distortion	Minimized None due to crossover fre- quency shifting.	same as passive	Distortion added. Crossover frequency and phasing of hi and lows shift with ac- tual impedance of speaker causing un- wanted frequencies going into wrong spakers and dulling of stereo image.
Crossover network distortion	<0.1% THD	<0.1% THD Coml. units 0.1 to 0.5%	Can be <0.1% THD with top quality components.
Reliability	Good—few components.	Has several fold more com- ponents with more chance for problems.	Good—few components.
Costs	Crossover: parts \$50 for 2 Ampl: Requires amplifier for each speaker.	Crossover: parts \$50 for 2, ready-built \$100-\$200 for 2. Ampl: Requires amplifier for each speaker.	Crossover: lowest cost Ampl: only 1 stereo required.
Time to build by amateur	2 hrs. for 2	20-40 hours. for 2	2 hrs. if coils ready built; add time if coils to be wound.
Insertion loss (—) or gain (+)	— 3.5 dB	0 to +3 dB typical Some types, —6 dB	Depends on quality (hi Q) of particular coils used. —0.1 to —2 dB typical.

4.0 from the treble, vs. the goal of 3.0. Theoretically, the total sound pressure level should then suffer a bit of a drop in the crossover region. Practically, this slight dip could not be measured in the total output from the speakers (audio generator input and microphone pickup) and certainly could not be detected by ear. The insertion loss was 3.6 to 3.2 dB (20 Hz and 20 kHz respectively).

As the text books state, distortion for the passive filter network should be practically nil. This was checked through the courtesy of a manufacturer's amplifier clinic and proved to be so. The filters were used between a Dynakit PAT-4 preamplifier and two Dynakit 120 amplifiers. The THD was measured at 2 volts output, which would fully load the amplifiers when feeding 16-ohm speakers. No difference could be read in the THD with and without the filters in the output.

In my setup, the amplifiers were

fed into the Altec-Lansing treble horns mentioned earlier and Klipschhorn bass corner horns. The defenders of the conventional crossover have pointed out that the electronic crossover (or filter) ahead of the amplifiers adds little or nothing to the damping of the bass speaker which is horn loaded like the Klipsch. Theoretically, this might be right. I have not had the opportunity yet to check this by A-B tests of conventional crossovers vs. filters with the horn-loaded speakers. Probably the differences are less prominent than with direct-radiating speakers. All I can say at this point is that the sound from the horns with the filters ahead of the amplifiers is superb.

If you have been following the interesting articles and letters to the editor in *AUDIO Magazine* for the last year and a half on this subject, you are pretty well posted on the pros and cons of electronic cross-

overs vs. conventional crossovers after the amplifiers.

This article presents another alternative, the passive filter networks *ahead* of the amplifiers. Comparing filters with electronic crossovers, it appears that there is a lot to be said for the filters, especially for the audiophile who wants to build the device himself with minimum time and cost. Advantages and disadvantages of the three alternatives are listed in Table I.

The debates continue on whether the sound is significantly better (and worth the cost) with the crossover ahead of the amplifiers. To anyone who has listened to an A-B test with direct radiating speakers, there is no doubt about the result being audibly better with crossovers ahead of the amplifiers. And for the audio buff who is determined to get the best in sound, an easy, economical, and reliable way to it is with the passive filters. Æ